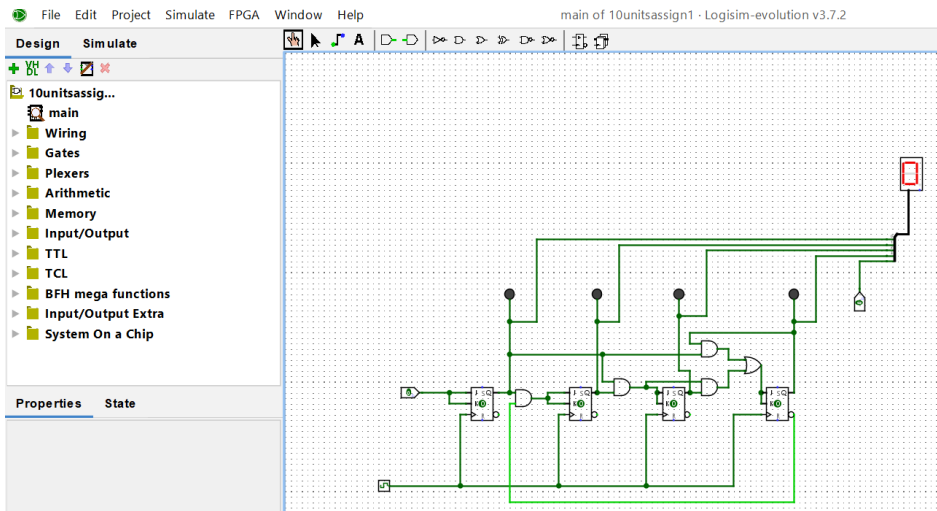



Lab 5 is about the preparation of assignment 1.

To start with, I created 2 types of counters.

1. 0-9 counters with a hexadecimal display.



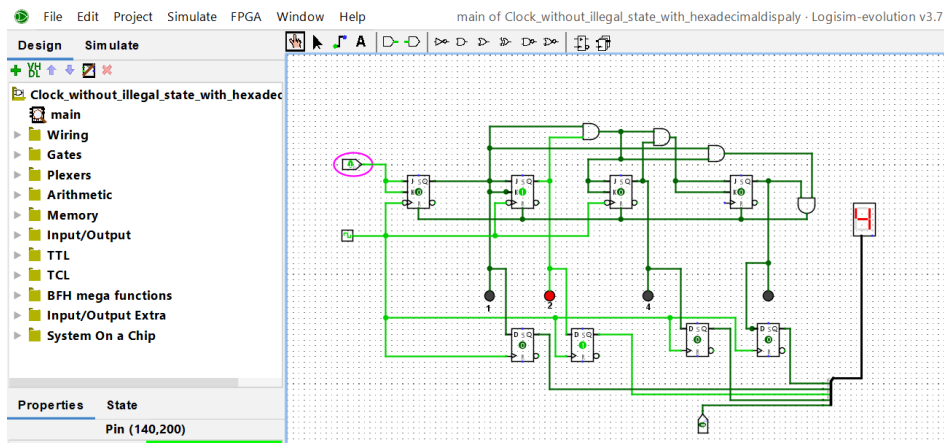2. 0-5 counters with a hexadecimal display.



3. Time to link both counters to make one while minute counter.

